
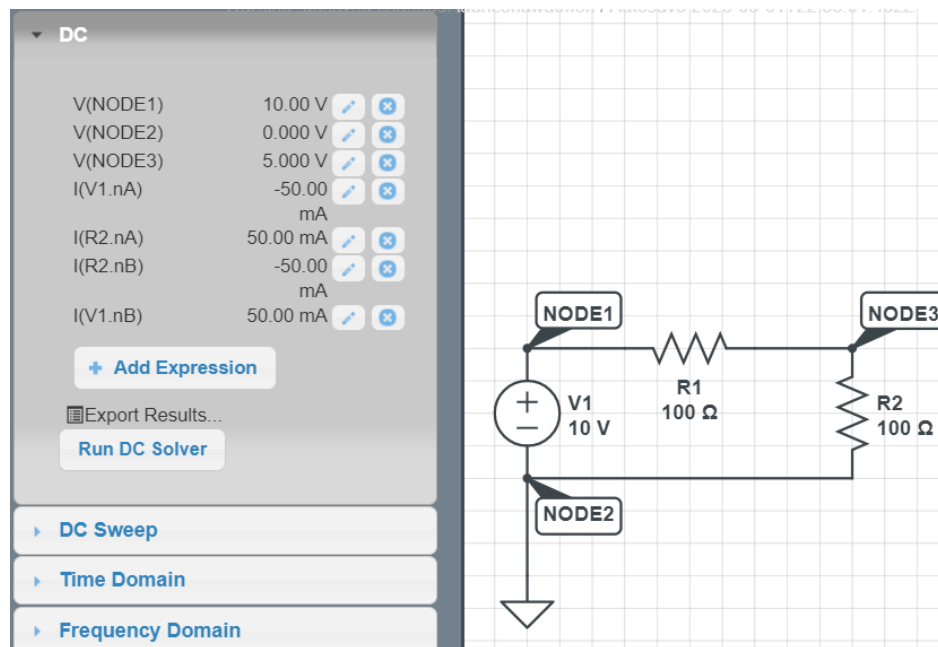


1c.

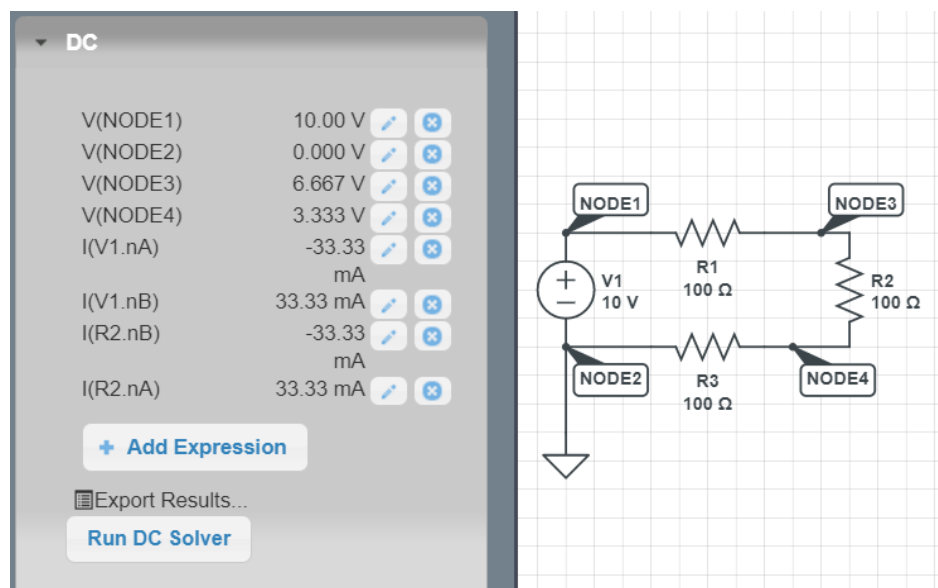


1d.




In a series circuit, the current through each of the components is the same, and the voltage across the circuit is the sum of the voltages across each component. In comparison to the case with two series resistors, adding a third series resistor reduces the amount of voltage flowing through each node and the overall current in the system.

2c.

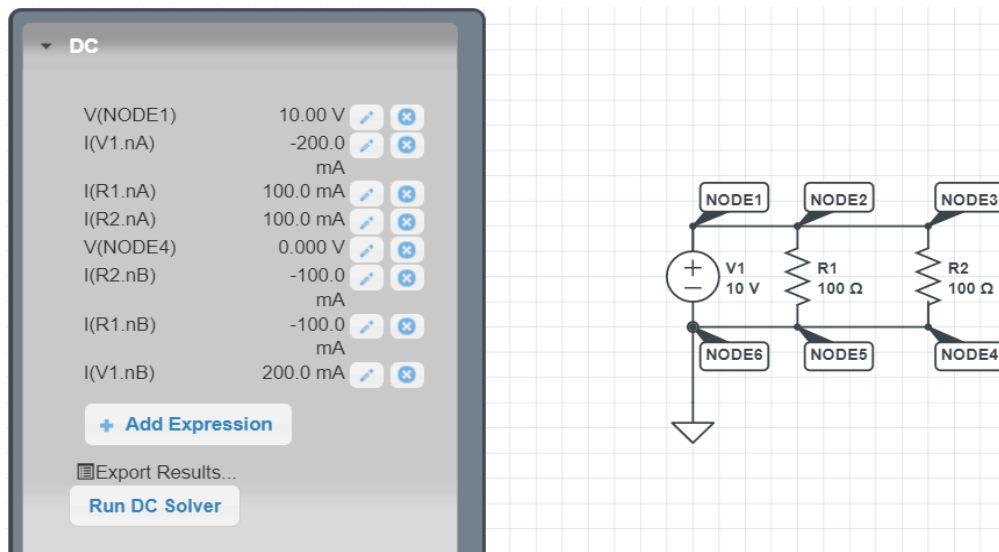


2d.

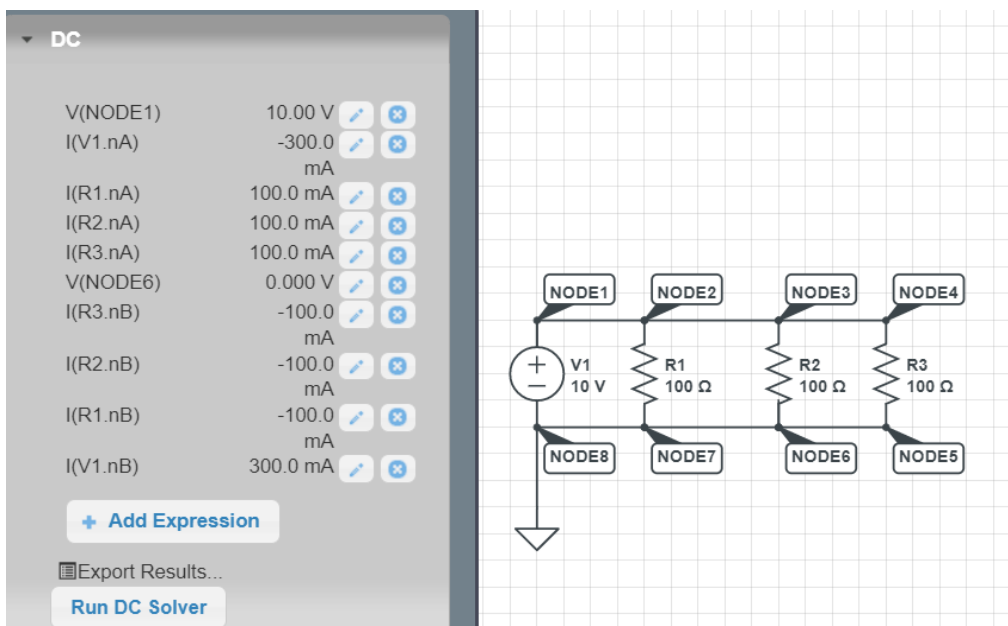

In a parallel circuit, the voltage across each of the components is the same, and the total current is the sum of the currents through each component. In comparison to the case with two parallel resistors, adding a third parallel resistor increases the current flowing into the voltage source while the voltage across each of the components stays the same.


3c.

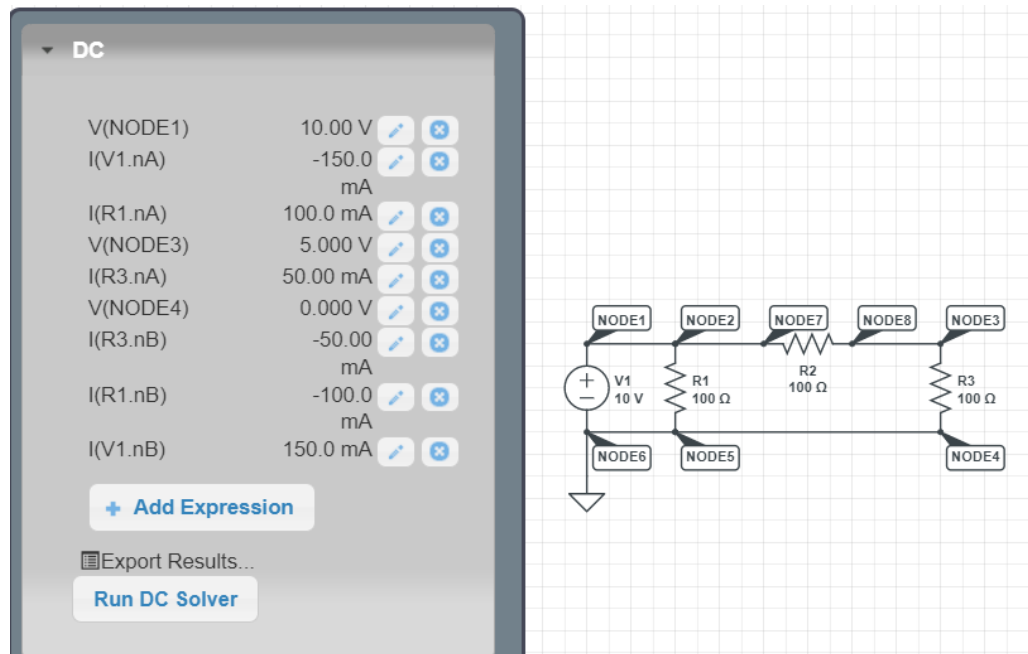



In the case of resistors only in series or only in parallel, either the current or voltage is constant. However, in the case of resistors in series and parallel, both the current and voltage are changing.

4a. $P = V^2/I = 10^2/100 = 1 \text{ W}$



4b.

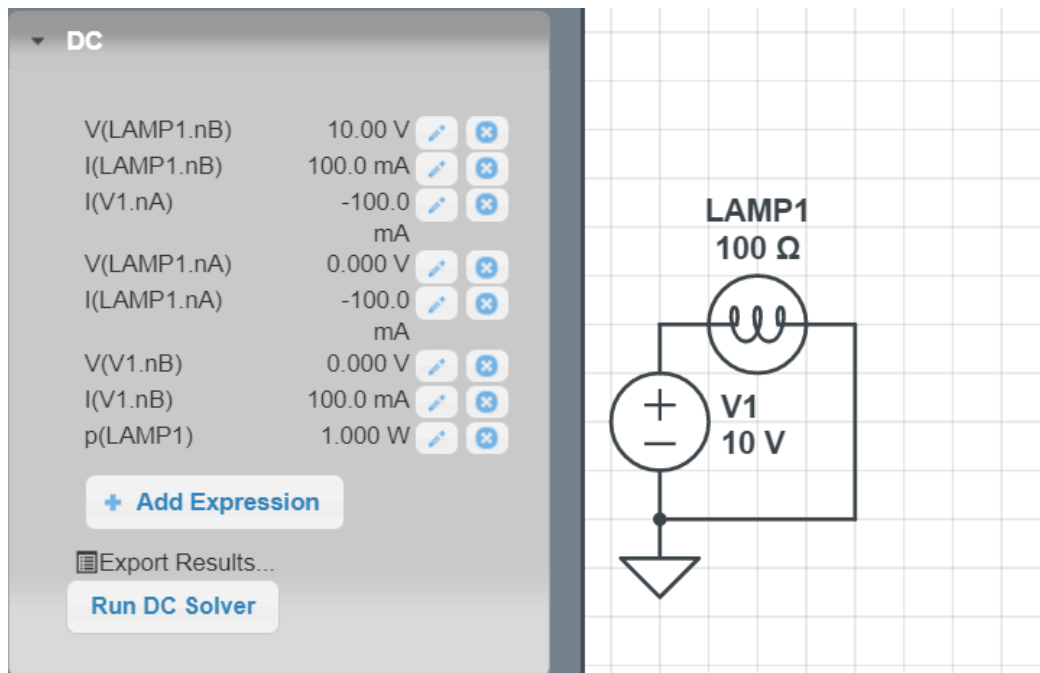



4c.

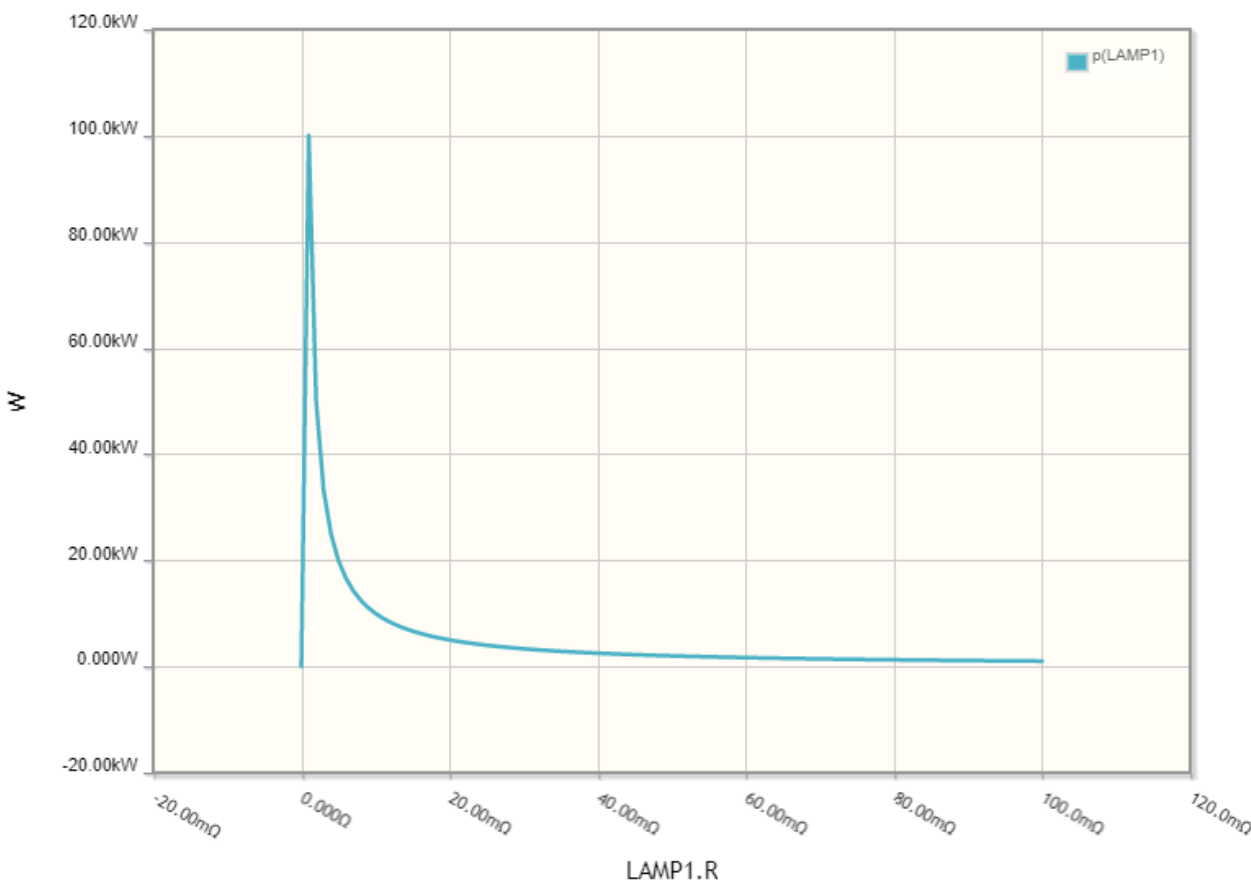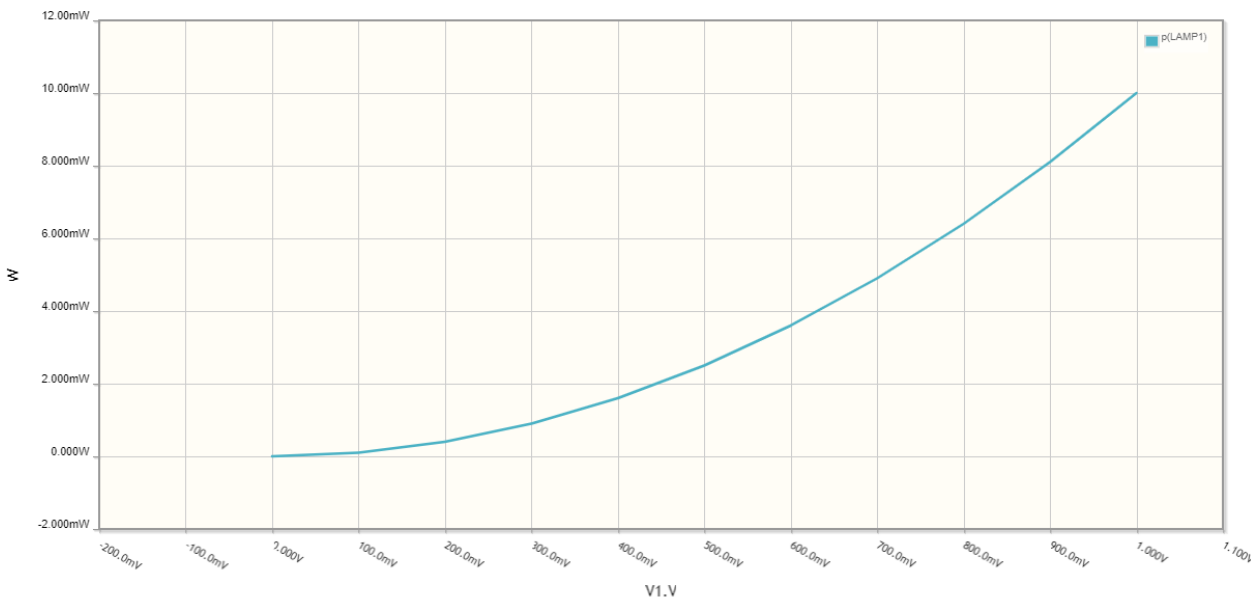

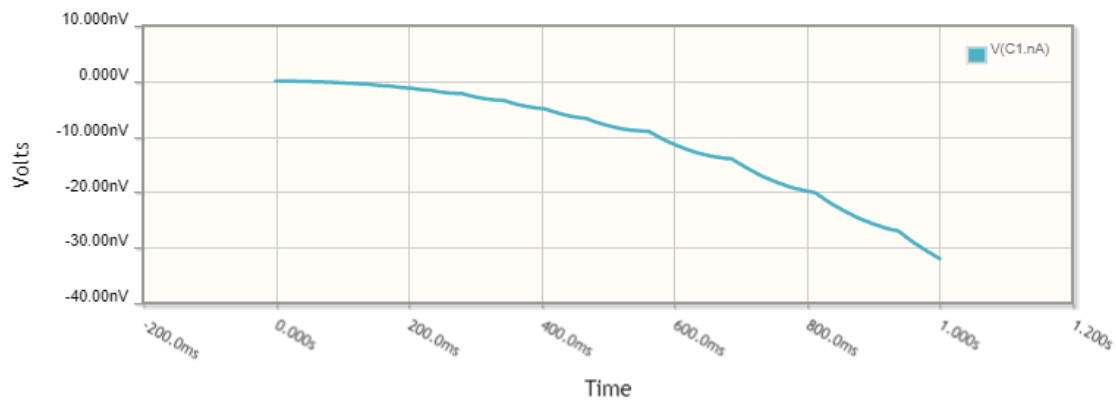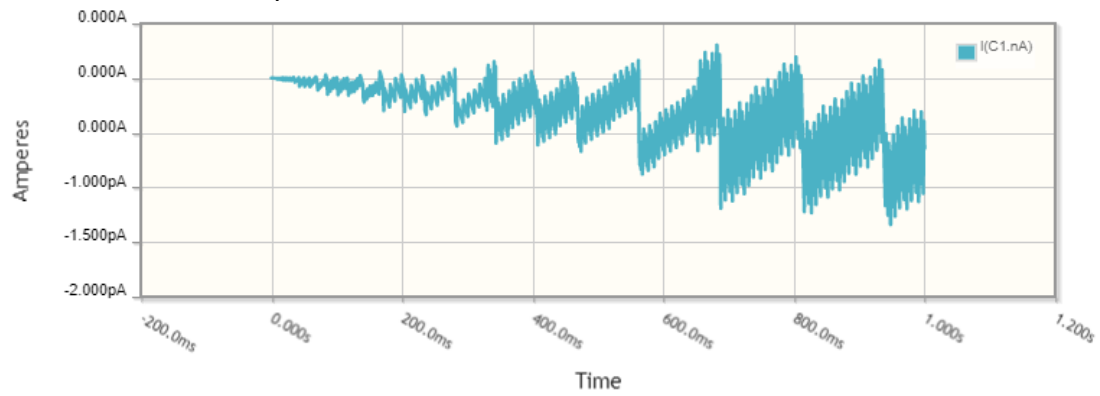
5b. 10 microfarad capacitor, sine current source



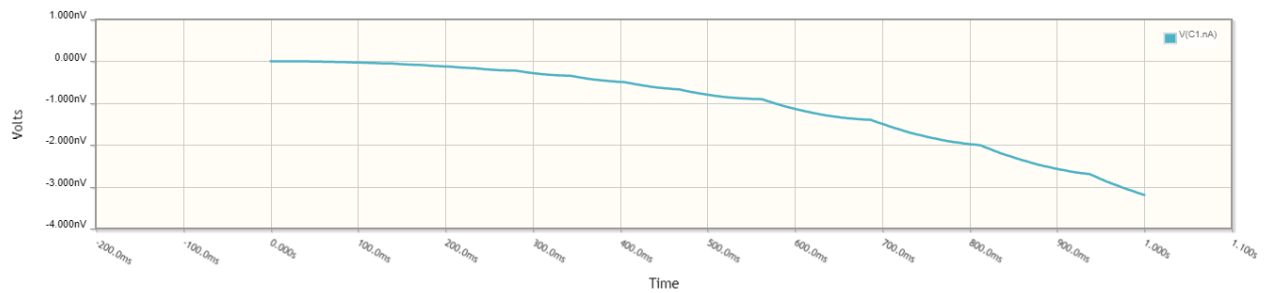
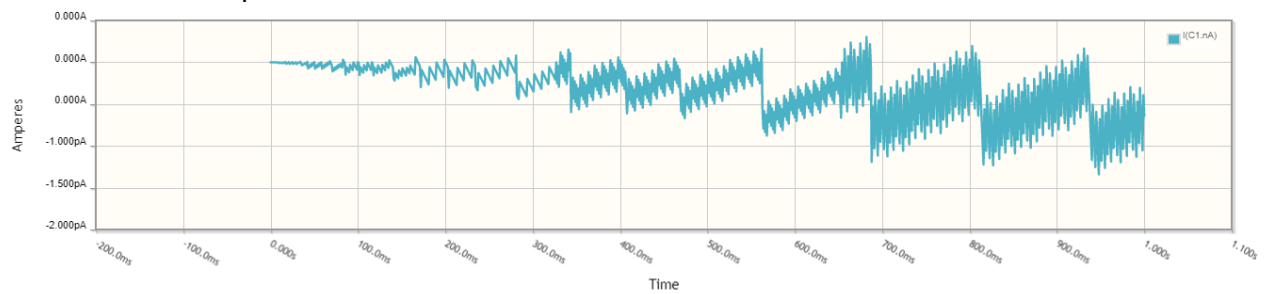
100 microfarad capacitor, sine current source



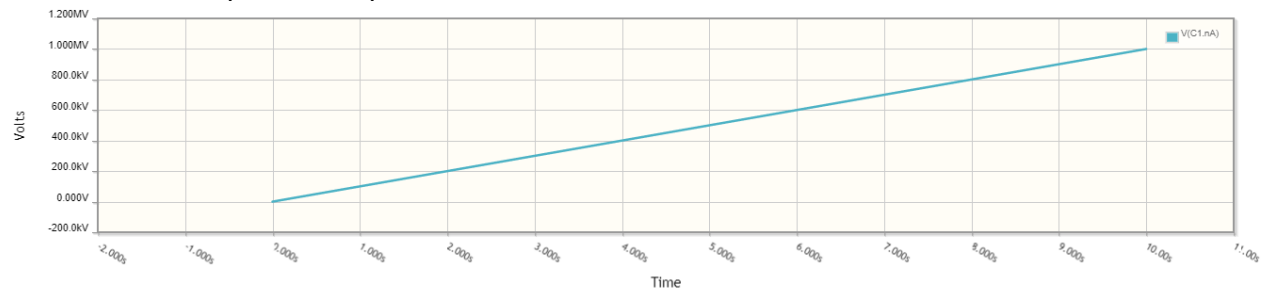10 microfarad capacitor, step current source





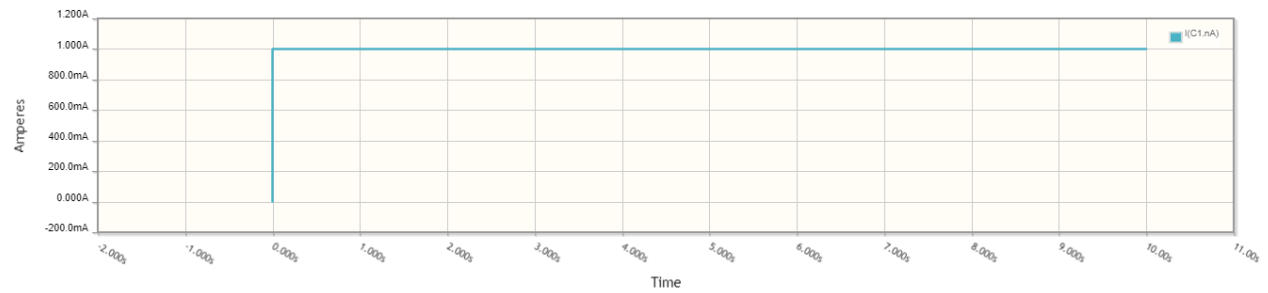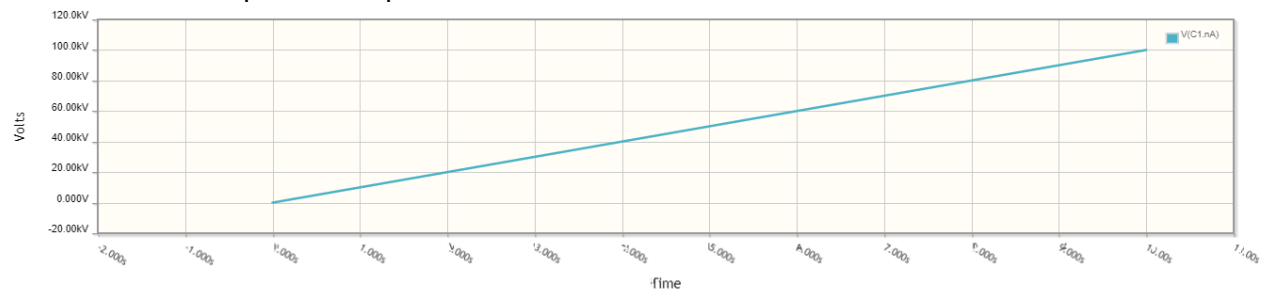100 microfarad capacitor, step current source





In either case, a change in capacitance caused the voltage to vary but had no effect on the current.

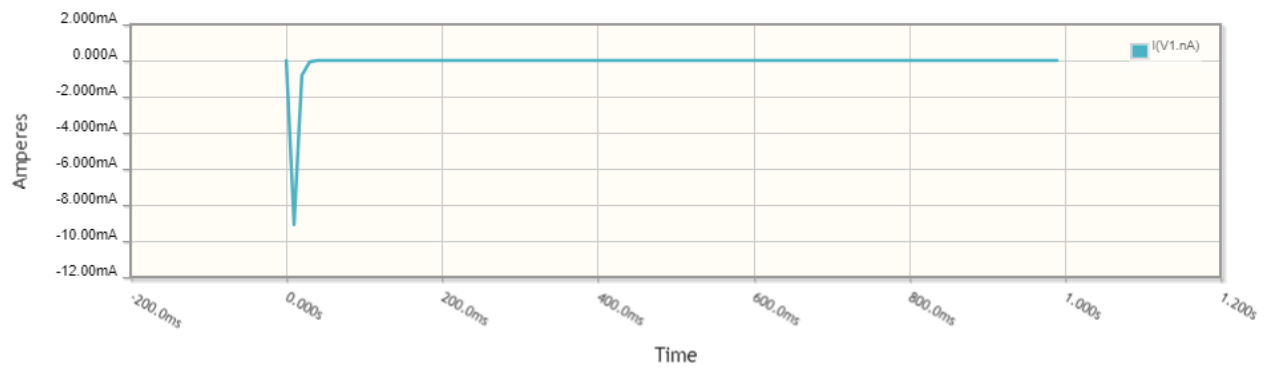
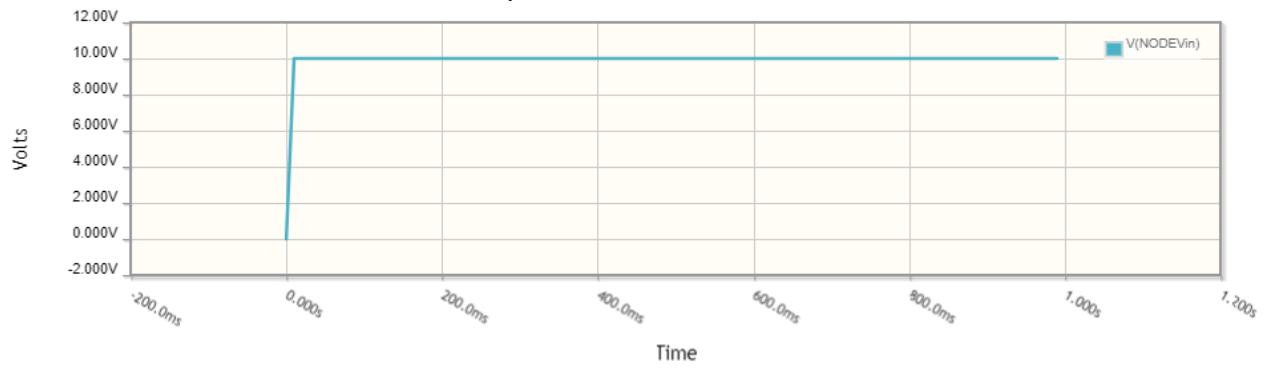
6b. 100 ohm resistor, 10 microfarad capacitor



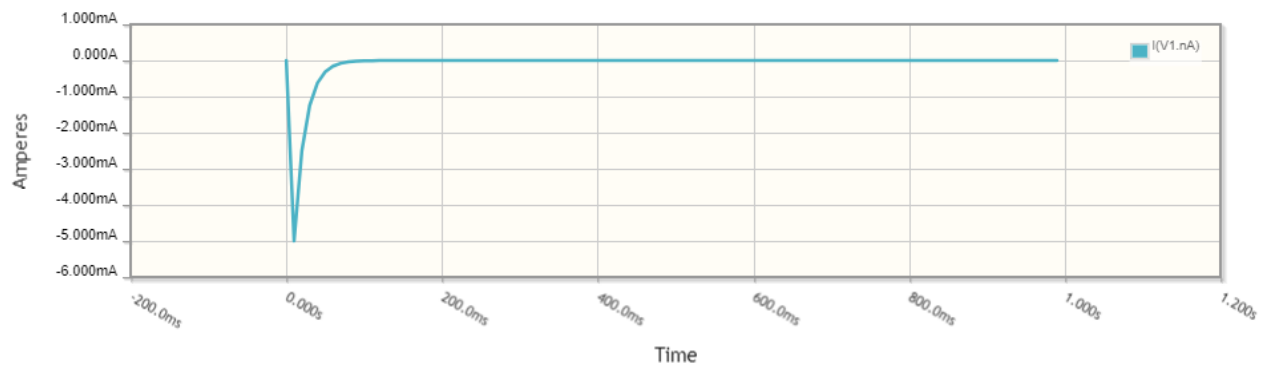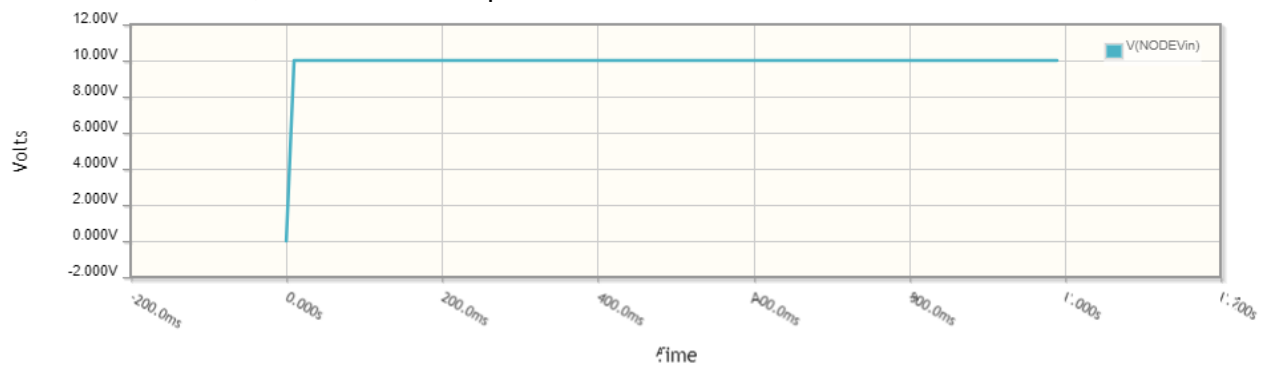
6c. 1 kohm resistor, 10 microfarad capacitor



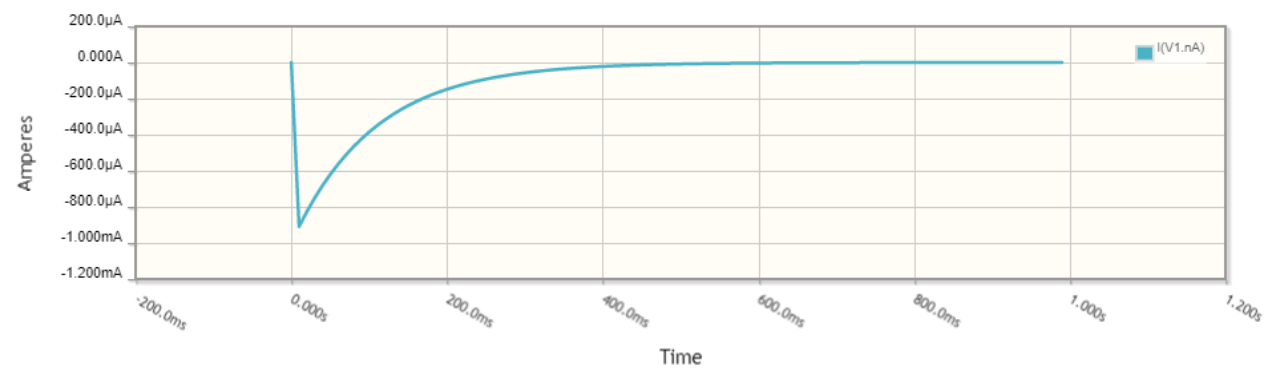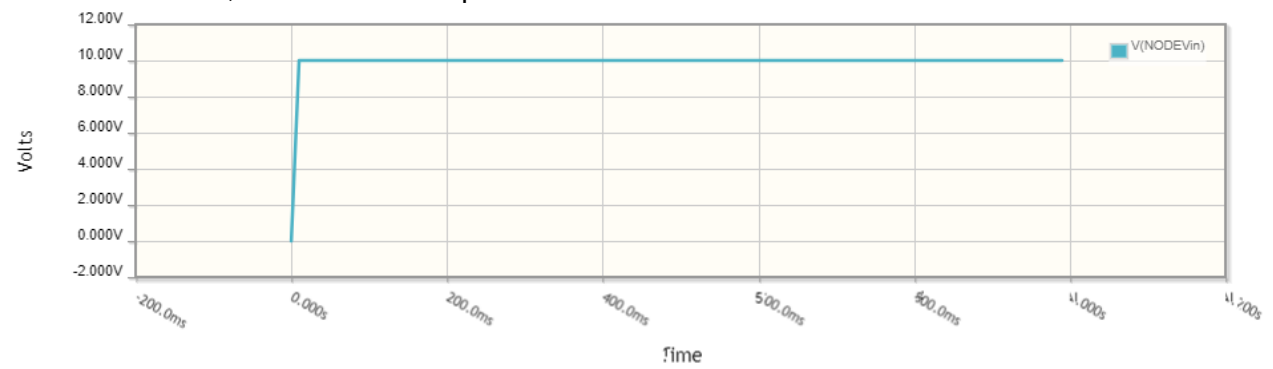
10 kohm resistor, 10 microfarad capacitor



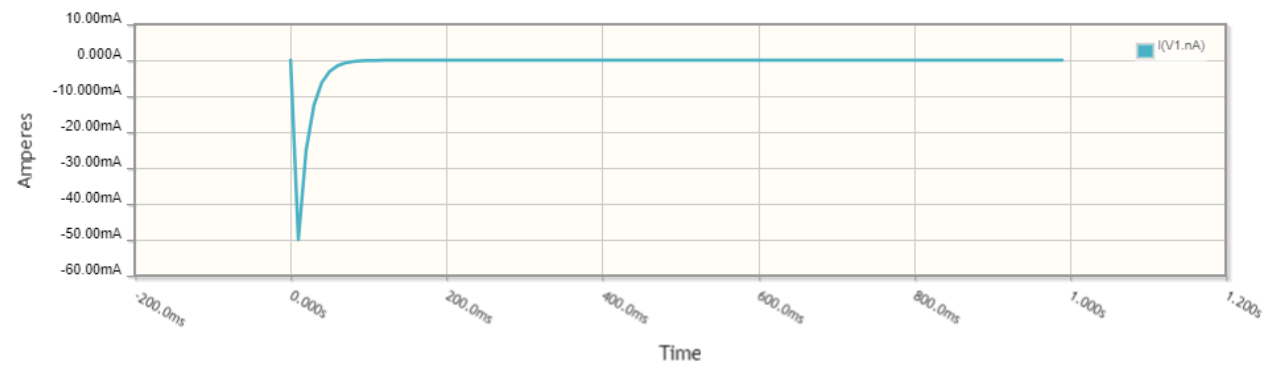100 ohm resistor, 100 microfarad capacitor




100 ohm resistor, 10 mF capacitor

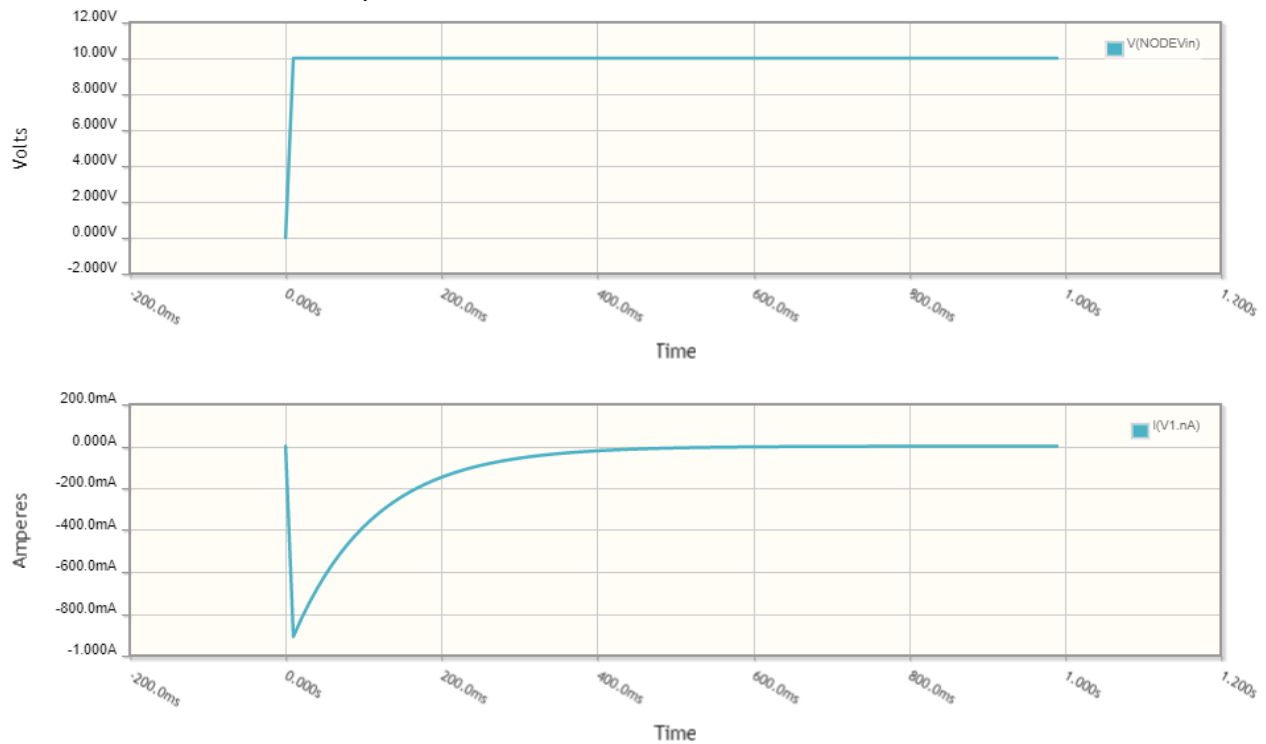



As you increase the resistance or capacitance in the system, the capacitor charges more slowly. “The characteristic time $\tau = RC$ tells you that the charging/discharging is slower with a larger resistor or capacitor. This makes sense, because a larger resistor impedes the flow of current; thus slowing the charging/discharging, and a larger capacitor holds more charge; thus requiring more time to charge” [1].

7a.


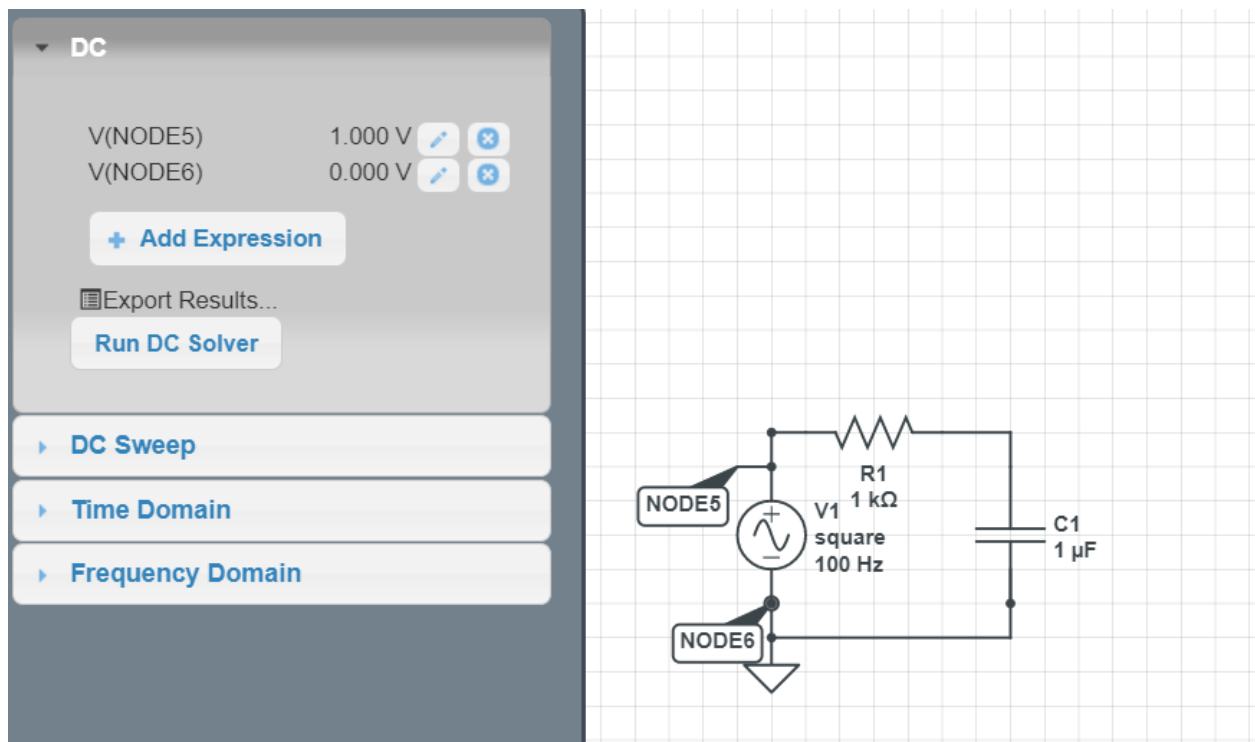


7b. 100 Hz frequency + 1 kohm resistor


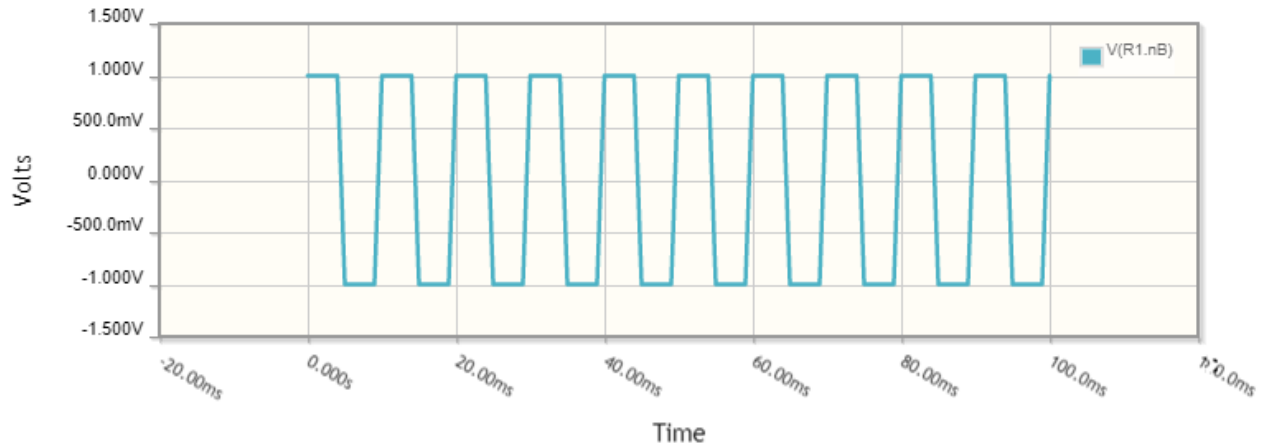


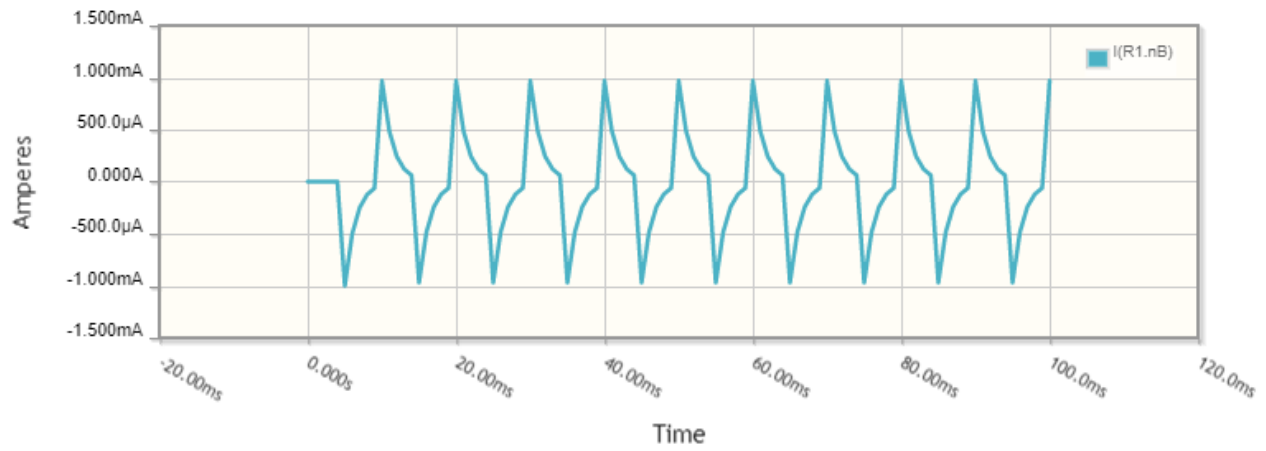


100 Hz frequency + 10 kohm resistor

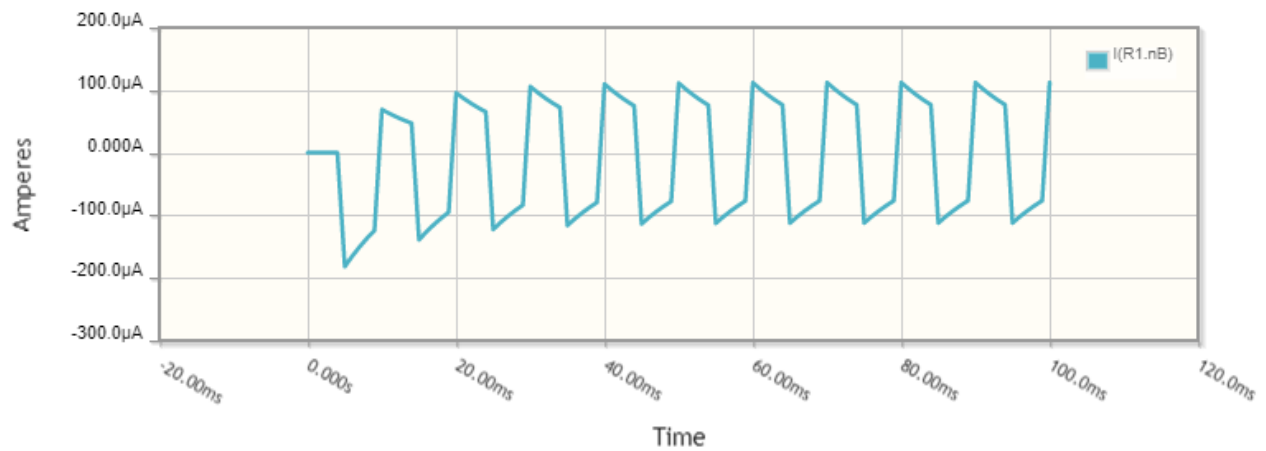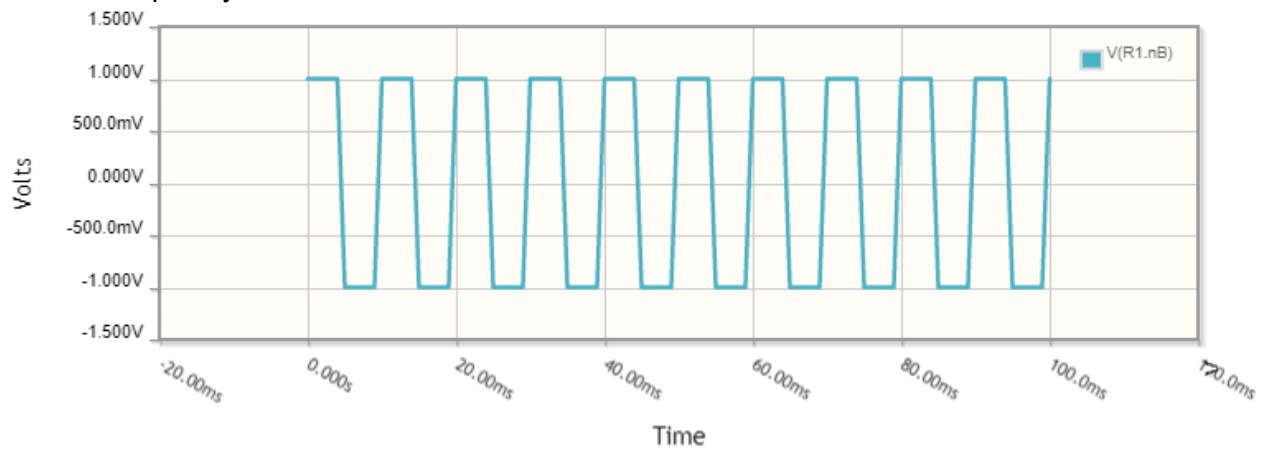


1 kHz frequency + 1 kohm resistor

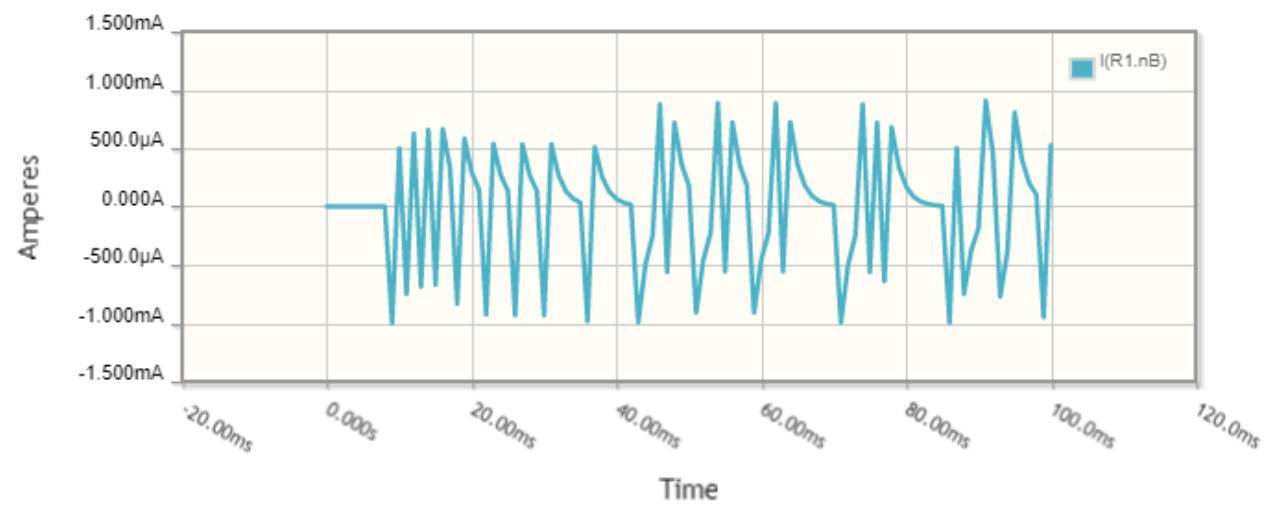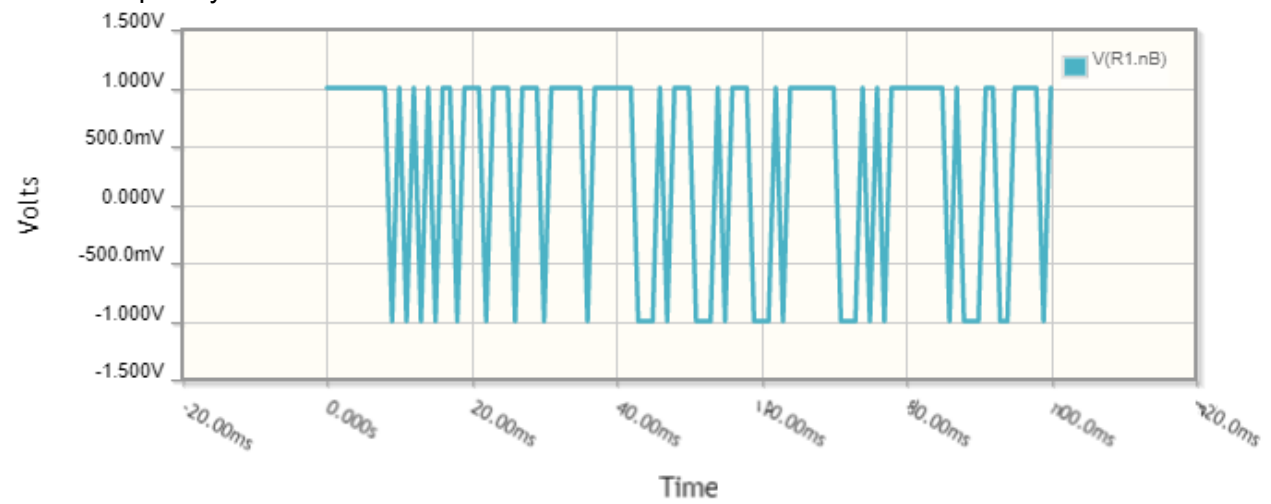

1 kHz frequency + 10 kohm resistor

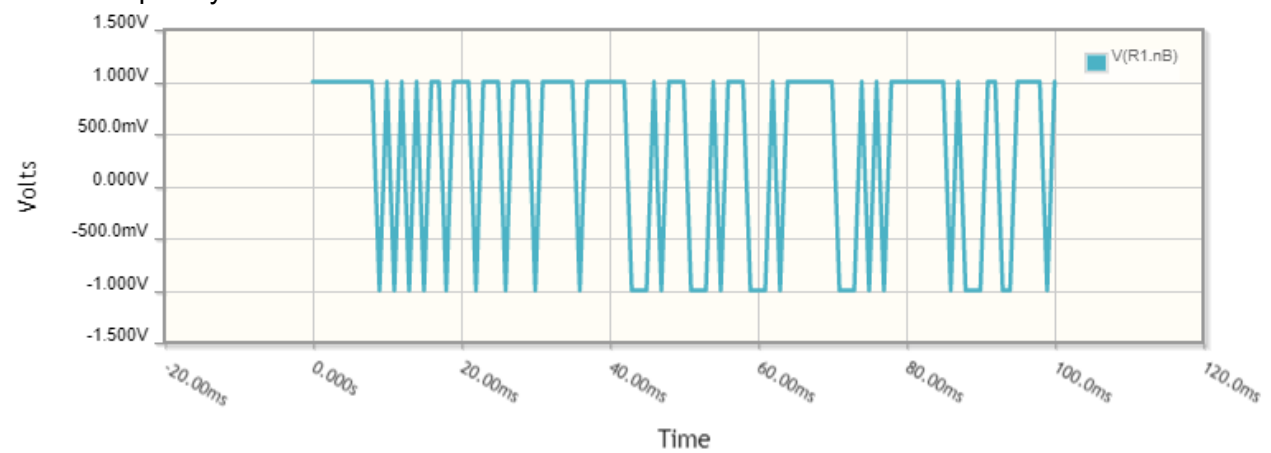

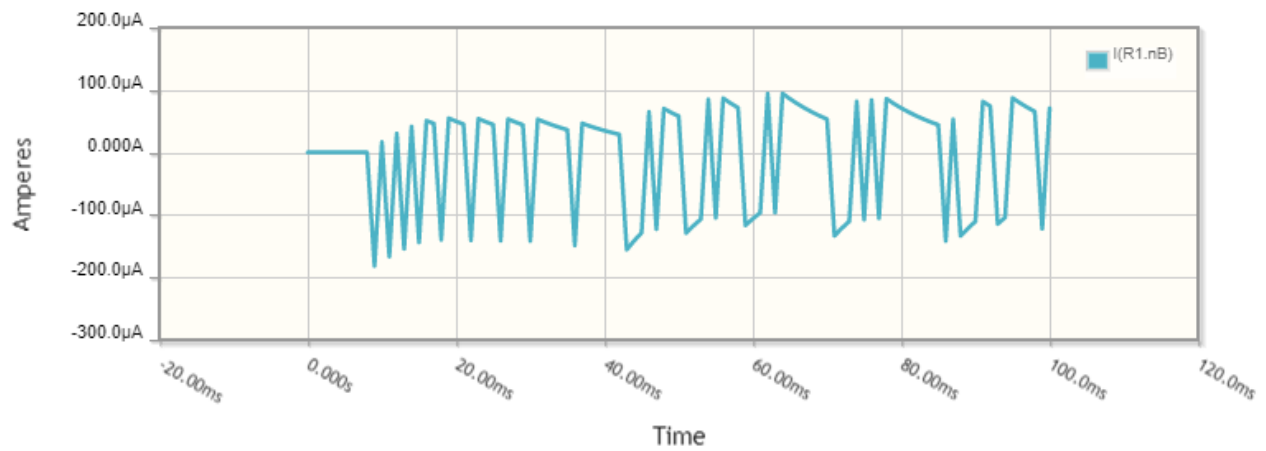

Changing the resistance does not affect the output voltage, it affects the current.

References

[1] <https://web.pa.msu.edu/courses/2000fall/phy232/lectures/rccircuits/rc.html>